

2018-Ph-H1-Q10

Section: Electricity

Topic: Current, PD, Power, Resistance

A 2.0 A current flows through a 4.0 Ω resistor.

What is the voltage across the resistor?

Solution:

Use Ohm's Law:

$$V = IR = 2.0 \times 4.0 = 8.0 \text{ V}$$

Answer: 8.0 V

Revision Tip:

Ohm's Law is fundamental: $V = IR$. Make sure you can rearrange it depending on which quantity is needed.