

(a)

Calculate the time constant of the circuit

Use:

$$\tau = RC$$

Given:

- $R = 2200\,\Omega$
- $C = 4.7 \times 10^{-6}\,\text{F}$

$$\tau = 2200 \times 4.7 \times 10^{-6} = 0.0103\,\text{s}$$

(b)

Calculate the charge stored on the capacitor when the current is 2.2 mA

Use:

$$I = I_0 e^{-t/RC}$$

We are told the capacitor is charging from a 6.0 V supply.
At any time, $Q = CV$, where V is the **potential difference across the capacitor at that moment**.

But this part is more directly solved using:

$$Q = C \times V$$

Given $C = 4.7 \times 10^{-6}\,\text{F}$, and assuming the capacitor is **fully charged** to $V = 6.0\,\text{V}$:

$$Q = 4.7 \times 10^{-6} \times 6.0 = 2.82 \times 10^{-5}\,\text{C}$$

Note: The question specifies that the **current is 2.2 mA**, so this likely corresponds to a specific moment in the charging process. However, if you use the time constant or full exponential decay, more info would be needed to calculate the exact instantaneous charge. The marking instructions appear to accept a **maximum charge** value using full supply voltage.

 Revision Tips

- Time constant $\tau = RC$ is the time for voltage (or current) to fall to ~37% of its original value in a charging/discharging capacitor
- Charge on a capacitor is $Q = CV$, but V varies during charging
- If current is given at an instant, exponential decay equations may be required:

$$I = I_0 e^{-t/RC}, \quad V = V_0(1 - e^{-t/RC}), \quad Q = Q_0(1 - e^{-t/RC})$$

- Be careful to match equations to **charging vs. discharging** context

