

 Section: Electricity

 Topic: Capacitors

(a)(i) Calculate the capacitance of the capacitor

✔ 3 marks

Given:

- $V = 5.7\text{ V}$
- $Q = 136.8\text{ mC} = 136.8 \times 10^{-3}\text{ C}$

Use the relationship:

$$C = \frac{Q}{V} = \frac{136.8 \times 10^{-3}}{5.7} = 0.0240\text{ F}$$

✔ Final answer:

24.0 mF

(a)(ii) Determine the absolute uncertainty in the capacitance

✔ 3 marks

Use percentage uncertainty method:

$$\text{Uncertainty in } Q = \frac{0.1}{136.8} \times 100 = 0.0731\% \quad \text{Uncertainty in } V = \frac{0.1}{5.7} \times 100 = 1.754\%$$

$$\text{Total \% uncertainty} = 0.0731 + 1.754 = 1.827\%$$

Now calculate absolute uncertainty:

$$\text{Absolute uncertainty} = \frac{1.827}{100} \times 0.0240 = 4.38 \times 10^{-4}\text{ F} = 0.00044\text{ F}$$

✔ Final answer:

$(0.0240 \pm 0.0004)\text{ F}$

(b) Calculate the estimated time taken for the capacitor to charge fully

✔ 2 marks

Use the relationship:

$$t = 5RC$$

Given:

- $R = 15\text{ k}\Omega = 15 \times 10^3\ \Omega$
- $C = 0.0240\text{ F}$

$$t = 5 \times 15 \times 10^3 \times 0.0240 = 1800\text{ s}$$

 Revision Tips

- Capacitors store charge: $Q = CV$
- Absolute uncertainty = (% uncertainty) × measured value
- Full charge time $\approx 5RC$, not just "RC"
- Work in SI units: F (farads), Ω (ohms), s (seconds)