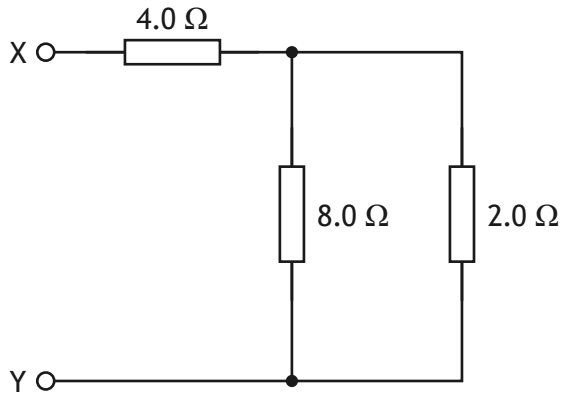


19. A circuit is set up as shown.



The total resistance between X and Y is

- A $1.1\ \Omega$
- B $1.7\ \Omega$
- C $4.6\ \Omega$
- D $5.6\ \Omega$
- E $14\ \Omega$.