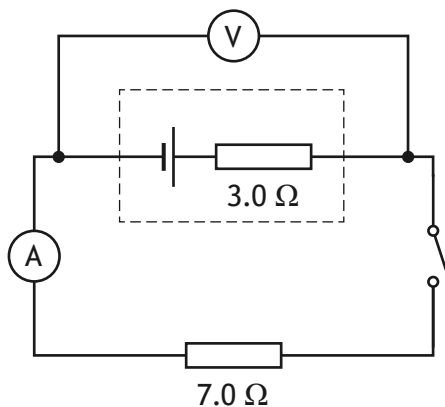


21. A $7.0\ \Omega$ resistor is connected to a cell as shown.



The internal resistance of the cell is $3.0\ \Omega$.

The switch is now closed.

The reading on the ammeter is $0.15\ \text{A}$.

Which row in the table shows the EMF of the cell and the reading on the voltmeter?

	EMF (V)	Reading on voltmeter (V)
A	0.45	1.05
B	1.05	0.45
C	0.60	0.45
D	1.50	1.05
E	1.50	0.45