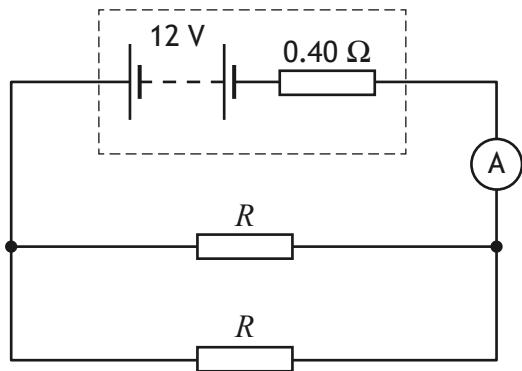


22. A battery has an EMF of 12 V and an internal resistance of  $0.40\ \Omega$ .

Two identical resistors each of resistance  $R$  are connected to the battery as shown.



The reading on the ammeter is 4.0 A.

The resistance  $R$  is

A  $0.77\ \Omega$

B  $2.6\ \Omega$

C  $3.0\ \Omega$

D  $3.4\ \Omega$

E  $5.2\ \Omega$ .