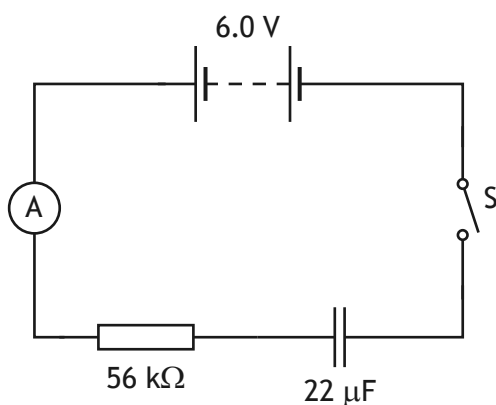


12. (a) A student sets up a circuit to investigate the charging of a capacitor.




The capacitor is initially uncharged. The student closes the switch and the capacitor takes 6.2 s to fully charge.

On the axes below, sketch a graph of current I against time t for the capacitor to fully charge.

Numerical values are required on both axes.

3

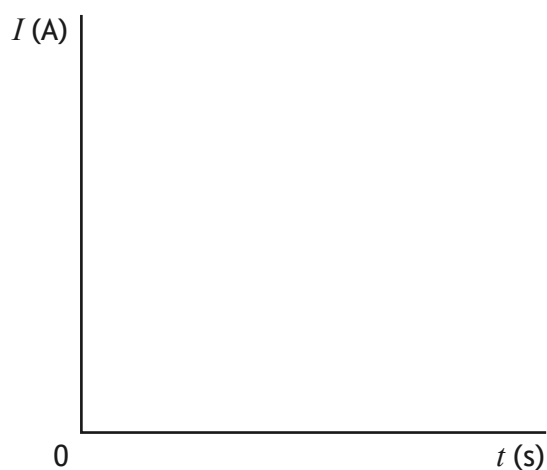

(An additional graph, if required, can be found on page 52.)


[Turn over

12. (continued)

MARKS

DO NOT
WRITE IN
THIS
MARGIN

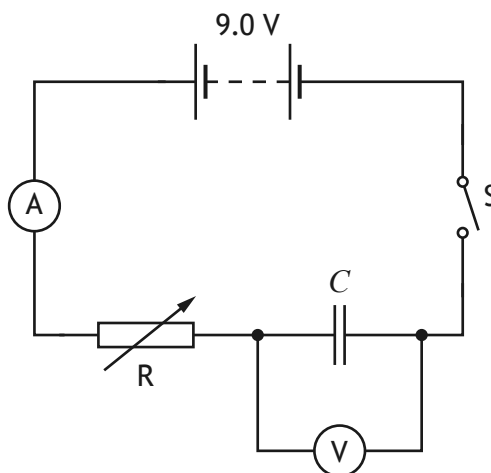- (b) In a second experiment, the student sets up a circuit to determine the capacitance C of a different capacitor.



The resistance of the variable resistor can be adjusted to maintain a constant charging current.

Initially, the capacitor is uncharged.

Switch S is closed and the capacitor begins to charge.

- (i) State whether the student should be increasing or decreasing the resistance of the variable resistor R to maintain a constant charging current.

Justify your answer.

2

- (ii) During the experiment, there is a constant charging current of $15 \mu\text{A}$. The capacitor takes 28 s to fully charge.

Calculate the charge stored on the capacitor when it is fully charged.

3

Space for working and answer



12. (b) (continued)

(iii) Calculate the capacitance C of the capacitor.

Space for working and answer

3

[Turn over

